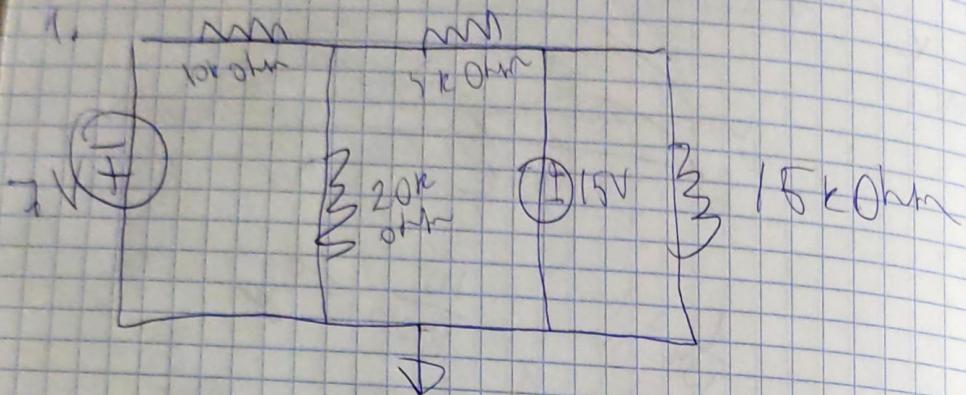


# Pre lab



1) switching off  $V_1$

$$R_{eq} = \frac{20 \cdot 5}{20+5} k = 4 \text{ kOhm}$$


$$I_{R_2} = \frac{1}{10k + 4k} = 0,5 \cdot 10^{-3} \text{ A}$$

$$I_{R_3} = \frac{2}{5 \cdot 10^3} = 0,4 \cdot 10^{-3} \text{ A}$$

$$I_{R_1} = \frac{2}{20 \cdot 10^3} = 0,1 \cdot 10^{-3}$$

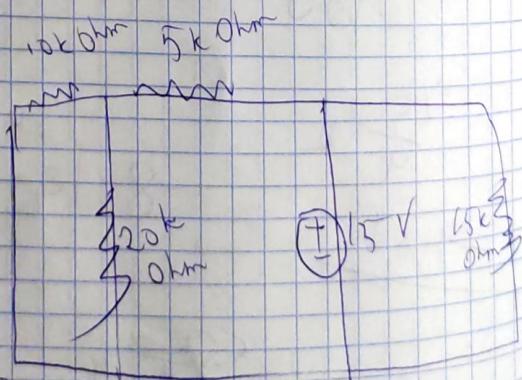2) switching off  $V_2$

$$I_{R_1} = \frac{15}{15k} = 1 \cdot 10^{-3} \text{ A}$$



$$I_{R_2} = \frac{15}{(20 \cdot 10^3) + 15k} = 1,3 \cdot 10^{-3} \text{ A}$$

$$I_{R_3} = \frac{9,5}{10k} = 0,95 \cdot 10^{-3} \text{ A}$$

$$I_{R_1} = \frac{9,5}{20k} = 0,475 \cdot 10^{-3} \text{ A}$$

3) Applying superposition pr.

$$I_{R_3} = 1,3 \cdot 10^{-3} + 0,4 \cdot 10^3 = 1,7 \cdot 10^{-3} \text{ A}$$


$$I_{R_2} = 0,95 \cdot 10^{-3} + 0,5 \cdot 10^{-3} = 1,45 \cdot 10^{-3} \text{ A}$$

$$I_{R_1} = 0,475 \cdot 10^{-3} - 0,1 \cdot 10^3 = 0,375 \cdot 10^{-3}$$

$$I_{R_4} = 10^{-3} \text{ A}$$


$R_{1,2} 1\text{k}\Omega$

2.

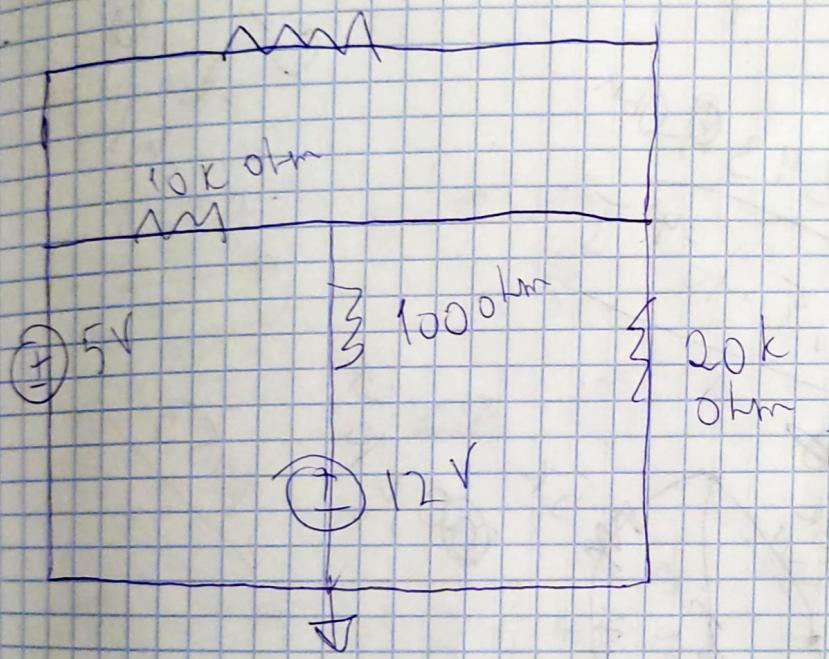

1) finding  $R_1$


1.1) switching off  $V_3$

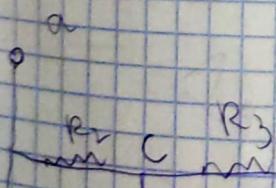

$$I_{R_2} = \frac{5}{10\text{k} + \frac{25\text{k} \cdot 10^2}{25+100}} = 495 \cdot 10^{-4} \text{ A}$$

$$I_{R_4} = \frac{0,5}{25\text{k}} = 0,02 \cdot 10^{-3} \text{ A}$$

1.2) Switching off  $V_2$

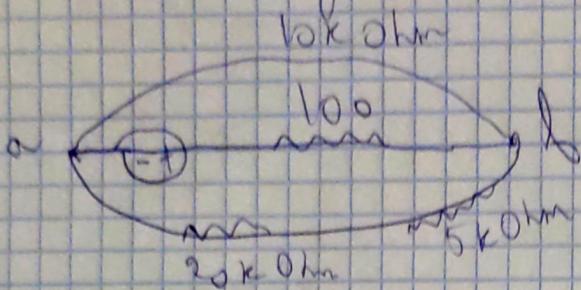

$$I_{R_2} = \frac{12 - 100 \cdot \left( \frac{12}{\frac{25 \cdot 10}{35} + 100} \right)}{10 \text{ k}} = \frac{11,835 \text{ V}}{10 \text{ k}} = 1,183 \text{ mA}$$


$$I_{R_3} = \frac{11,835}{25 \text{ k}} = 4,7 \cdot 10^{-4} \text{ A}$$

1.3) Using Superposition pr.

$$I_{R_2} = 0,02 \cdot 10^{-3} - 0,118 \cdot 10^{-4} = -8,8 \cdot 10^{-5} \text{ A}$$

$$I_{R_3} = 4,7 \cdot 10^{-4} + 4,95 \cdot 10^{-4} = 9,65 \cdot 10^{-4}$$


1.4) finding  $R_{eq}$

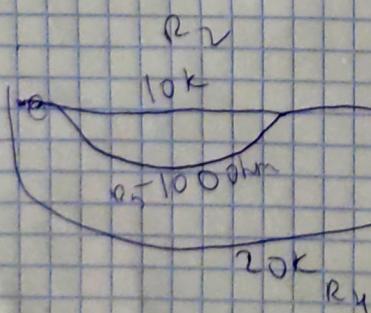


$$R_{eq} = \frac{\left( \frac{R_2 \cdot R_3}{R_2 + R_3} + R_4 \right) R_4}{\left( \frac{R_2 \cdot R_3}{R_2 + R_3} + R_3 \right) + R_4} = 4 \text{ k}$$

$$\begin{aligned}
 3) V & \text{ or } R_1 \\
 a - C_5 & = 9,8 - V \\
 b - C & = -4,865 V \\
 a - B & = 4,935 V \\
 V_{R1} & = 0,2 \cdot 4,935 = 0,987 V
 \end{aligned}$$

Finding  $R_4$  using Nor-Ohm

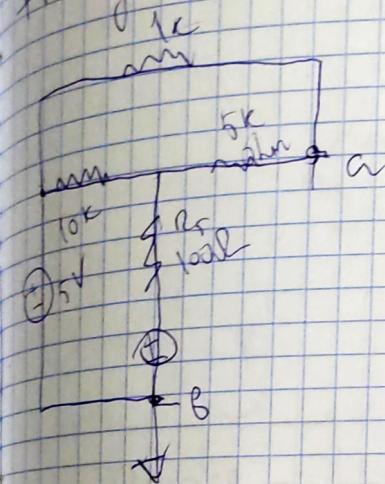

1.) Switching off  $V_2$

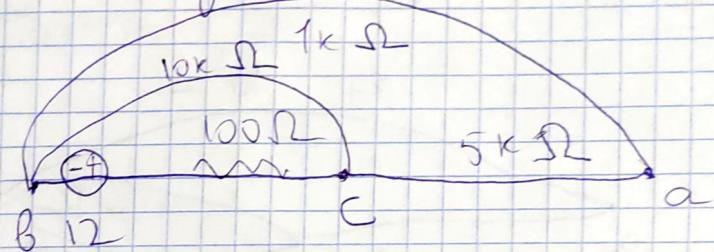

$$12 - V_{R5}$$

$$R_{eq} = \left( \frac{10 + 6}{10 + 6} \right) k = \frac{15}{4} k$$

$$R_{eq} = \frac{15}{4} k + 100 = 3850 \Omega$$

$$V_{R5} = \frac{12}{3850} \cdot 100 = 0,31 V$$

$$I_{R1} = \frac{11,69}{6 k} \approx 2 \cdot 10^{-3} A$$

$$R_{eq} = \frac{6 + 10}{10} k = \frac{15}{4} k$$

$$R_{eq} = 3850 \Omega$$

$$I_{R1} = 100 \cdot \left( \frac{5}{3850} \right) = 0,13 V$$

$$I_{R1} = \frac{4,87 V}{6 k} = 0,81 \cdot 10^{-3} A$$

1.3) Using Superposition pr.


$$I_{R_1} = 2 \cdot 10^3 - 0,81 \cdot 10^3 = 1,19 \cdot 10^3 \text{ A}$$

$$a - c = 119 \text{ V}$$

$$c - b = 5 \text{ V}$$


$$a - b = 6,2 \text{ V}$$

1 ii) Finding  $R_{eq}$ .

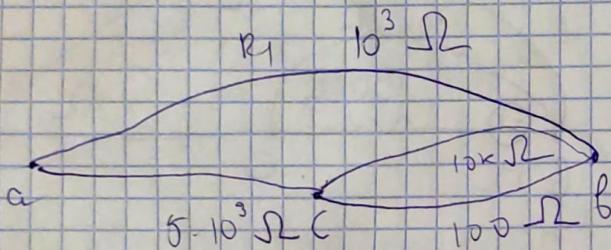

$$R_{eq} = \frac{10^3 \cdot (5 \cdot 10^3 + (\frac{10^4 \cdot 100}{10k+100}))}{10^3 + (5 \cdot 10^3 + (\frac{10k \cdot 100}{10k+100}))} \approx 8350 \Omega$$
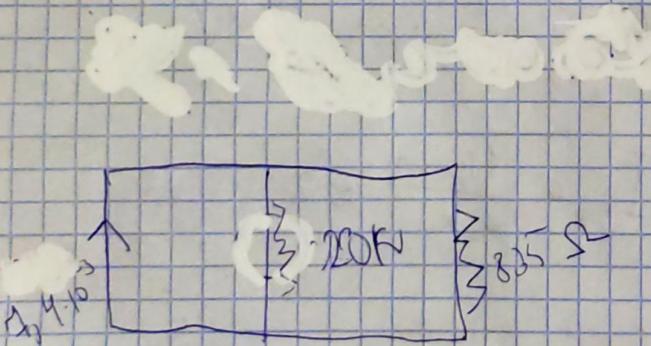
$$I_N = \frac{6,2}{8350} = 7,4 \cdot 10^{-3} \text{ A}$$



$$V_{R_{eq}} = 297 \cdot 10^{-6} \cdot 20 \cdot 10^{-3} = 5,94 \cdot 10^{-3} = 5,94 \text{ V}$$


$$20 \cdot 10^{-3} \cdot 11 = 835 \cdot 11$$

$$L_1 = \frac{835 \cdot 7,4 \cdot 10^{-3}}{20835} = 297 \cdot 10^{-6} \text{ A}$$


# Post Lab

$B_3, R_1$  using Thevenin

$R_2$  and  $R_4$  using Norton

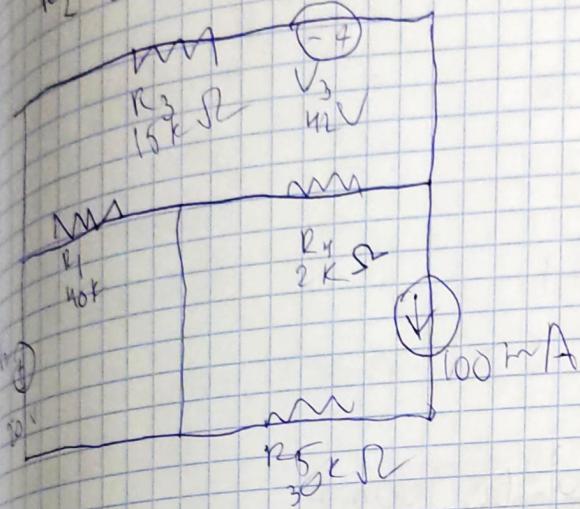

1) finding  $R_3$

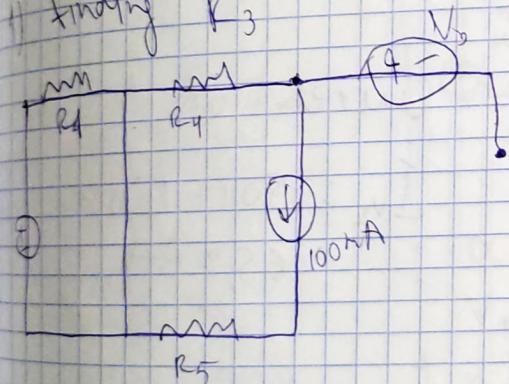

2) Switching off  $V_2$

$$10 \cdot 10^3 \cdot L_1 = 18 \cdot 10^3 \cdot C_2$$

$$58 \cdot 10^3 \cdot C_1 = 1800$$

$$I = \frac{900}{29} \cdot 10^{-3} \approx 31 \cdot 10^{-3} A$$

3) find  $V_1$

$$b - c = 31 \cdot 10^{-3} \cdot 40 \cdot 10^3 \approx 1241 V$$

$$c - d = 2 \cdot 10^3 \cdot 100 \cdot 10^3 \approx 200 V$$

$$d - a = 42 V$$


4)  $R_T$

$$\left( \frac{4 \cdot 18}{58} k + 2 k \right) \parallel \left( \frac{4 \cdot 18}{58} k + 2 k \right) \parallel 1483 k$$

$$b - a = 1483 V$$

$$5) \frac{1483V}{15k + 15,72} = 50,1 \text{ mA}$$

finding  $R_1$

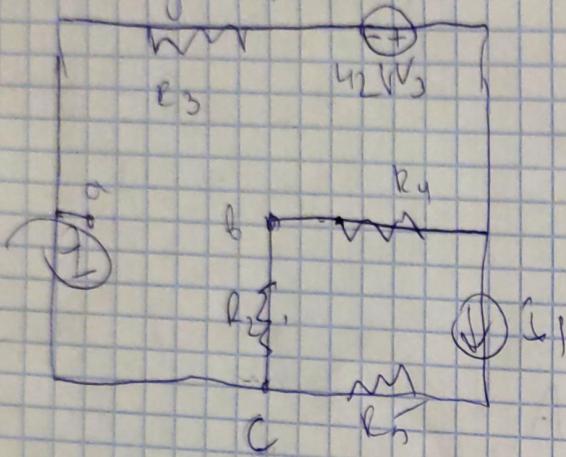

$$15U_1 = 20R_2 = 0, \quad I_1 = 100 \text{ mA}$$

$$35R_2 = 1500$$

$$I_1 = 13 \text{ mA}$$

$$a - c = 20V$$

$$b - c = 7,2$$

$$a - b = 7,2 V$$

$$V_T = -7,2 V$$

finding  $R_{eq}$


$$R_{eq} = \frac{17,18}{35k} = 487,5 \Omega$$

$$I_{A_1} = \frac{7,2}{48,75k} = 15,8 \text{ mA}$$

current on  $V_1$

$$I_{V_1} = 50,1 + 15,8 = 65,9 \text{ mA}$$

and  $R_4$  using Norton

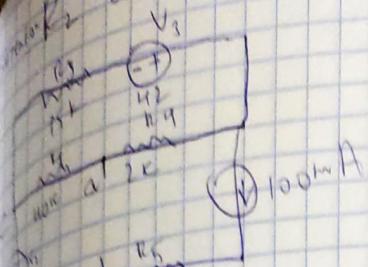

$$R_2 R_4 = 15k\Omega$$

$$5k\Omega \cdot 15k\Omega = 1500$$


$$I_1 = 26,3 \text{ mA}$$

$$c-a = 40E. 26,3 \text{ mA} = 1053 \text{ V}$$

$$c-b = 20 \text{ V}$$

$$b-a = 1033 \text{ V}$$

$$V_{Th} = 1033 \text{ V}$$

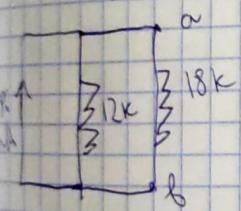

$$12k R_1 = 18k R_2$$

$$30k I_1 = 1033$$


$$I_1 = 34,4 \text{ A}$$

2) Finding  $R_{Th}$

$$R_{Th} = \frac{40 + V_{Th}}{5} = 12k$$

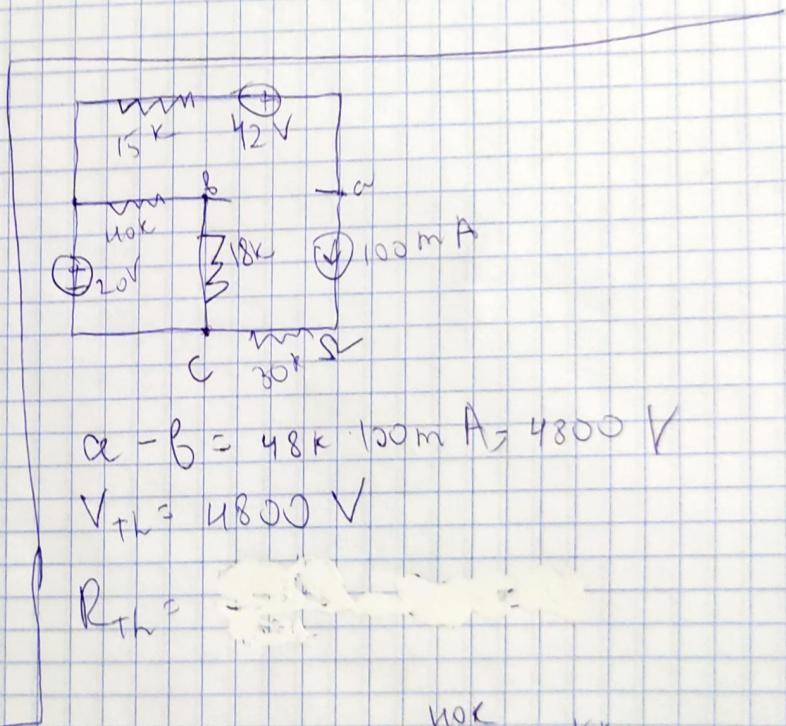3)  $I_N$

$$I_N = \frac{1033}{12k} = 86 \text{ mA}$$



$$a-b = 48k \cdot 100 \text{ mA} = 4800 \text{ V}$$

$$V_{Th} = 4800 \text{ V}$$

$$R_{Th} = \dots$$

